

# CIRCUIT CONNECTIONS

## Ultra sonic sensor circuit diagram :

gnd= gnd

Eco = digital 11

Trige = digital 10

Vcc = 5v

| Sensor | Arduino    |
|--------|------------|
| GND    | GND        |
| ECO    | DIGITAL 11 |
| TRIGE  | DIGITAL 10 |
| VCC    | 5V         |

## Lcd display circuit diagram :

Gnd = gnd

Vcc = 5v

SDA = A4

SCL = A5

| Sensor  | Arduino |
|---------|---------|
| GND     | GND 5V  |
| VCC SDA | A4 A5   |
| SCL     |         |
|         |         |

## PIR sensor :

Vcc = 5v

Input = Digital 3

Gnd = Gnd

Led positive = 13

Led negative = gnd

| Sensor         | Arduino   |
|----------------|-----------|
| VCC            | 5V        |
| INPUT          | DIGITAL 3 |
| GND            | GND       |
| LED - POSITIVE | 13        |
| LED - NEGATIVE | GND       |

## Touch sensor :

Vcc= 5v

GND = GND

SIG = Digital 7

Led positive = 13

Led negative = gnd

| Sensor         | Arduino    |
|----------------|------------|
| VCC            | 5V         |
| GND            | GND        |
| SIG            | DIGITAL 7  |
| LED – POSITIVE | DIGITAL 13 |
| LED – NEGATIVE | GND        |

## DTH11 sensor :

Vcc – 5v

Data- D2

GND – GND

| Sensor | Arduino   |
|--------|-----------|
| VCC    | 5V        |
| DATA   | DIGITAL 2 |
| GND    | GND       |

## LED Blinking :

| Sensor         | Arduino   |
|----------------|-----------|
| LED – POSITIVE | DIGITAL 7 |
| LED – NEGATIVE | GND       |

## BUZZER Blinking :

| Sensor            | Arduino   |
|-------------------|-----------|
| BUZZER – POSITIVE | DIGITAL 7 |
| BUZZER – NEGATIVE | GND       |